



NATIONAL UNIVERSITY OF MODERN LANGUAGES

FACULTY OF ENGINEERING AND COMPUTING
Computer Science Department

Assignment # 1

Course Title: Applied Physics

Course Code: MPTH-111

Semester & Section: 1st

Course Teacher: Mr. Tehseen Hussain

Total Marks: 10

Submission Date: 1 week

Student Name _____ Reg No. _____

Assignment Title: Kirchhoff's Law and Series/Parallel Combination of resistors

Q. No. 1: PLO 1, CLO 1

Marks (10)

a) Using series/parallel reductions, **determine** the equivalent resistance seen by the source in Figure 1. Also find all the voltages and currents?

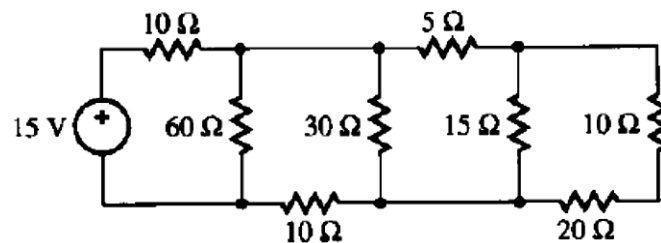


Figure 1

b) **Apply** the kirchoff's voltage law(KVL) to find all voltages, currents and the power by all resistors and source shown in Figure 2?

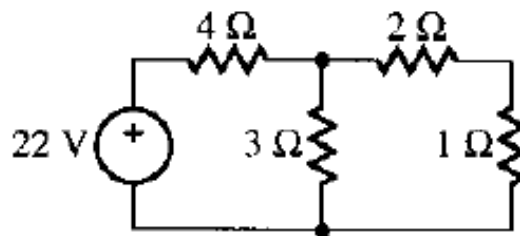


Figure 2